

Tablas de Verdad


ALGORITMOS Y PROGRAMACIÓN

Patricio Sierra



Anáhuac
Mayab


Circuito 1

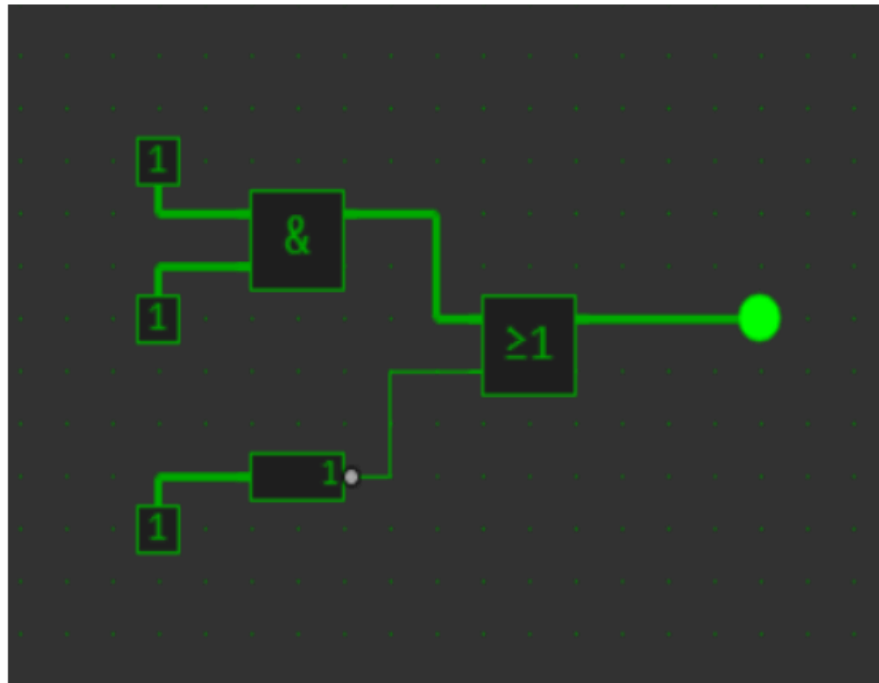

← 1. $(p \text{ AND } q) \text{ OR } (\text{NOT } p)$


p	q	p AND q	NOT q	$(p \text{ AND } q) \text{ OR } (\text{NOT } q)$
V	V	v	f	v
V	F	f	v	v
F	V	f	f	f
F	F	f	v	v

Circuito 2

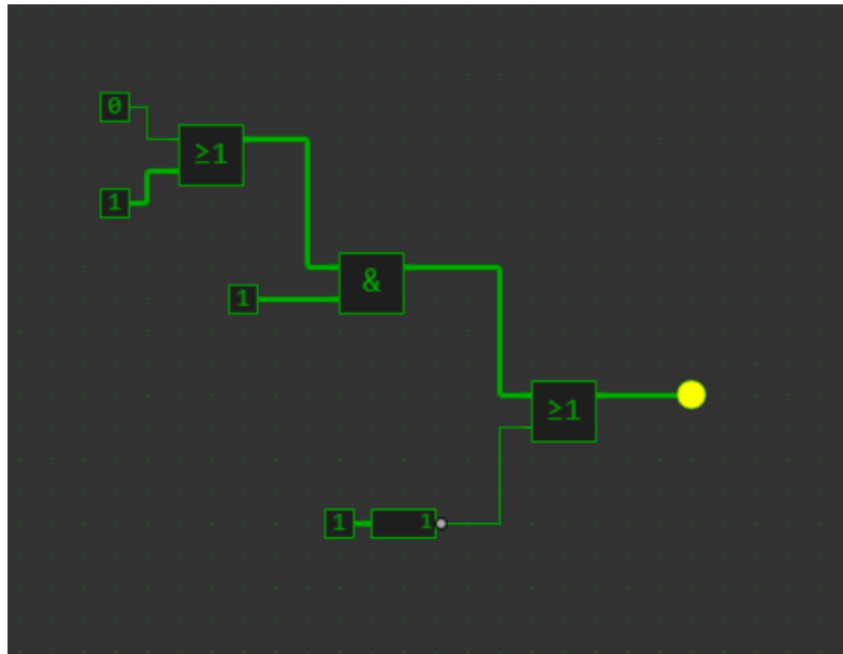


p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	v	f	f
V	F	v	f	f
F	V	v	f	f
F	F	f	v	f

Circuito 3

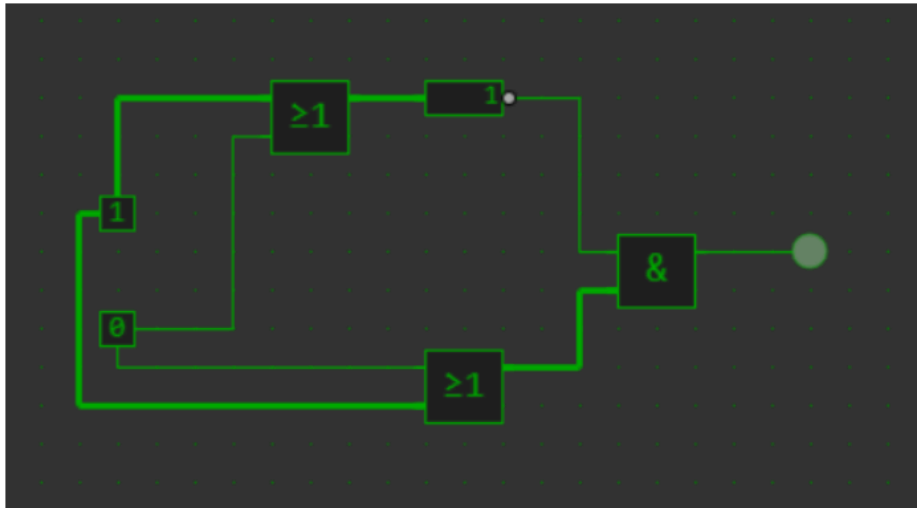

p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	V	F	F
V	F	V	F	F
F	V	V	F	F
F	F	F	V	F

Circuito 4

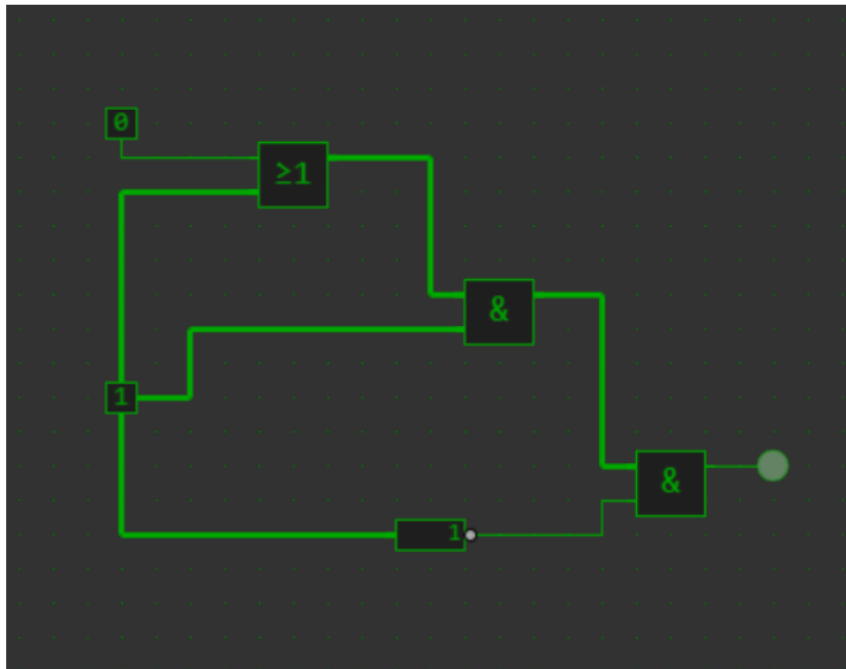

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] AND (NOT q)
V V	V	V	F	F
V F	V	F	V	F
F V	V	V	F	F
F F	F	F	V	F